

Lab 4: This program multiplexes the number 5,6,7,8 on the four 7-segment display (using assembly language programming). You must also sketch the circuit diagram in your lab report.

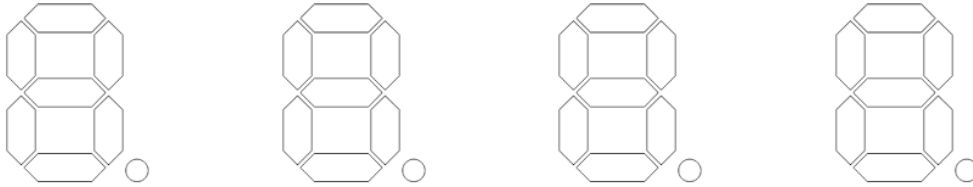


Fig: 7 -segment display